

Below is a concise walkthrough of how that slide (and its scribbled notes) derive the circuit for a 3-bit input ($X_2X_1X_0$) whose 3-bit 2's-complement output ($Y_2Y_1Y_0$) equals “input -2 .”

1. Truth Table Construction

Because the input is only 3 bits (0 through 7 in decimal), you list each input and compute (input $- 2$) in 3-bit 2's-complement:

| Decimal Input | $X_2X_1X_0$ | (input $- 2$) in decimal | (input $- 2$) in 3-bit 2's-comp | $Y_2Y_1Y_0$ |
|---------------|-------------|---------------------------|----------------------------------|-------------|
| 0 | 000 | -2 | 110 | 110 |
| 1 | 001 | -1 | 111 | 111 |
| 2 | 010 | 0 | 000 | 000 |
| 3 | 011 | 1 | 001 | 001 |
| 4 | 100 | 2 | 010 | 010 |
| 5 | 101 | 3 | 011 | 011 |
| 6 | 110 | 4 | 100 | 100 |
| 7 | 111 | 5 | 101 | 101 |

From this table:

- $Y_2 = 1$ for input decimal $\{0, 1, 6, 7\}$
 - $Y_1 = 1$ for input decimal $\{0, 1, 4, 5\}$
 - $Y_0 = 1$ for input decimal $\{1, 3, 5, 7\}$
-

2. Setting Up the K-Maps

A Karnaugh map for 3 inputs can be arranged in a 2×4 or 4×2 grid. A common layout is:

- Columns labeled by (X_2, X_1) in Gray code: 00, 01, 11, 10
- Rows labeled by $X_0 = 0$ and $X_0 = 1$

You create three separate K-maps, one for each output bit Y_2, Y_1, Y_0 . Below is a conceptual sketch for Y_2 . The same grid pattern is repeated for Y_1 and Y_0 .

| | X2 X1 | | | |
|------|-------|----|----|----|
| | 00 | 01 | 11 | 10 |
| X0=0 | ? | ? | ? | ? |
| X0=1 | ? | ? | ? | ? |

(a) K-Map for Y_2

- Mark a 1 in the cells corresponding to $(X_2X_1X_0)$ in $\{000, 001, 110, 111\}$.
- Notice that these cells form two 2×1 vertical “blocks” that combine to a larger grouping if your K-map arrangement is standard.
- The minimal Sum of Products (SOP) from that grouping is:

$$Y_2 = (X_2'X_1') + (X_2X_1).$$

Equivalently, $Y_2 = 1$ when X_2 and X_1 are equal—often called the “equivalence” function $X_2 \leftrightarrow X_1$.

(b) K-Map for Y_1

- From the truth table, Y_1 is 1 for $\{000, 001, 100, 101\}$.
- All of those have $X_1 = 0$, so the simplified form is:

$$Y_1 = X_1' = \neg X_1.$$

(c) K-Map for Y_0

- From the truth table, Y_0 is 1 for $\{1, 3, 5, 7\}$ in decimal, i.e., whenever $X_0 = 1$.
- So, immediately:

$$Y_0 = X_0.$$

3. Final Expressions

Putting it all together, the final minimal SOP expressions for “input -2 ” in 3-bit 2’s-complement are:

$$Y_2 = X_2'X_1' + X_2X_1,$$

$$Y_1 = X_1',$$

$$Y_0 = X_0.$$

These three outputs correctly yield (input -2) for any 3-bit input $X_2X_1X_0$.

Key Takeaways

1. **Truth Table:** Enumerate all inputs (0–7), then subtract 2 in 3-bit 2’s-complement.
2. **K-Maps:**
 - Each output bit gets its own 3-input K-map.
 - Label in Gray code so adjacent cells differ by only one bit.
3. **Simplification:**
 - Identify the largest adjacent groupings of 1-cells in each K-map.
 - The resulting minimal SOP reveals the neat patterns:
 - Y_2 is an equivalence function of (X_2, X_1) .
 - Y_1 is simply $\neg X_1$.
 - Y_0 is simply X_0 .

Hence, the scribbles you see on the slide show how to fill the K-maps (grouping 1-cells) and arrive at those nicely reduced Boolean expressions.